





# Open electronics:

From sensor to readout

**Ecole Polytechnique PHY564#2 2017** 

Yvan BONNASSIEUX, Christophe de LA TAILLE, Jean-Charles VANEL

Organization for Micro-Electronics desiGn and Applications

### **Measurement setups**



Each measurement needs a tool...



0 1 2 3 4 5


mm : 0.1 €

Higgs Boson 1 G€

#### **Image sensors**



CMOS technology for cameras

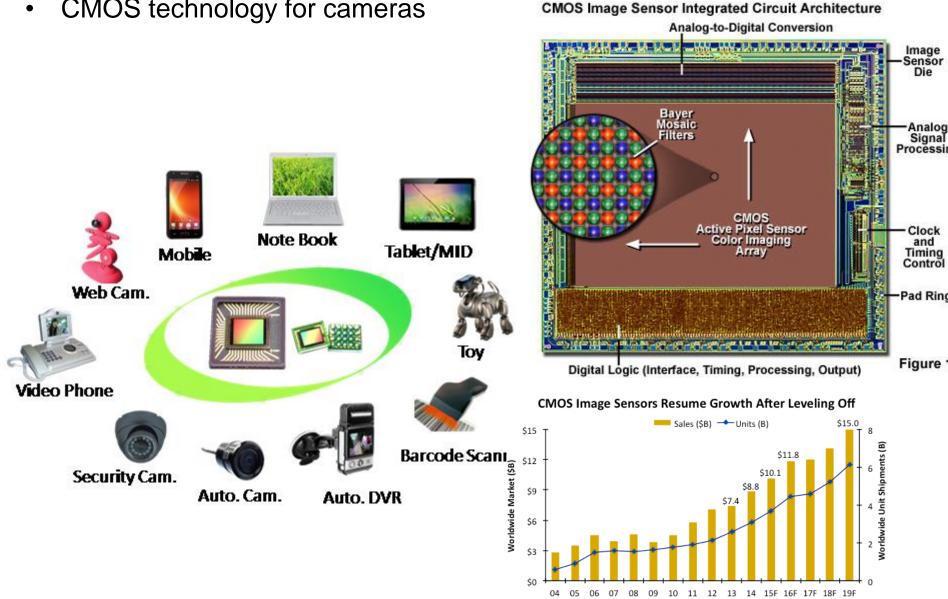


Source: IC Insights

#### **Particle detectors**




Measurement of tracks and energy

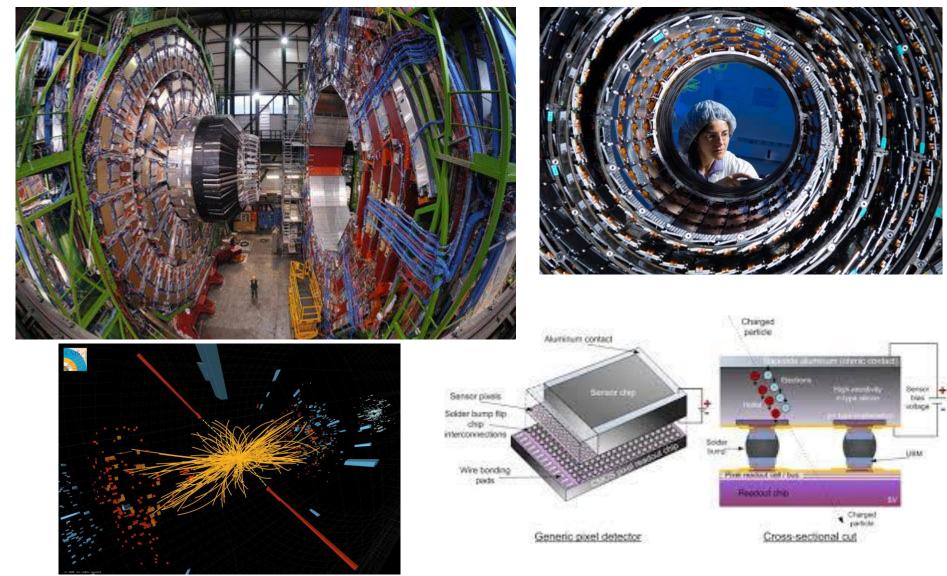
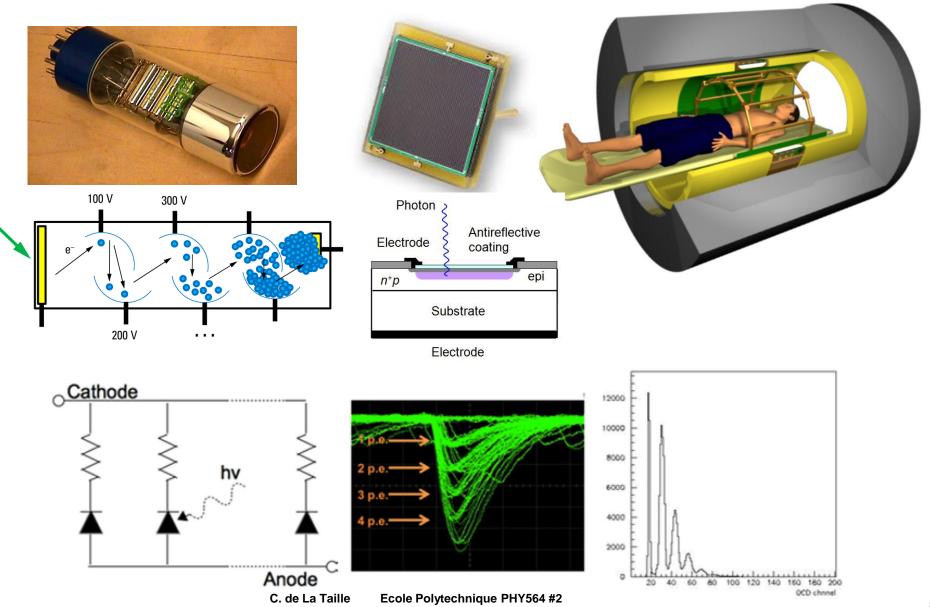
# Single photon sensors




Photomultipliers, silicon photomultipliers


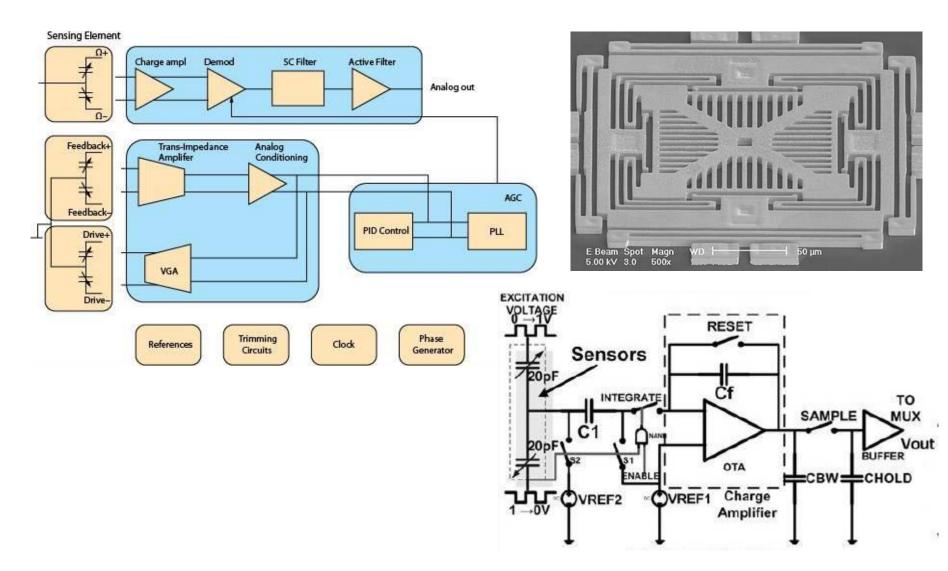
#### **MEMS** readout




Accelerometer readout : variation of capacitance





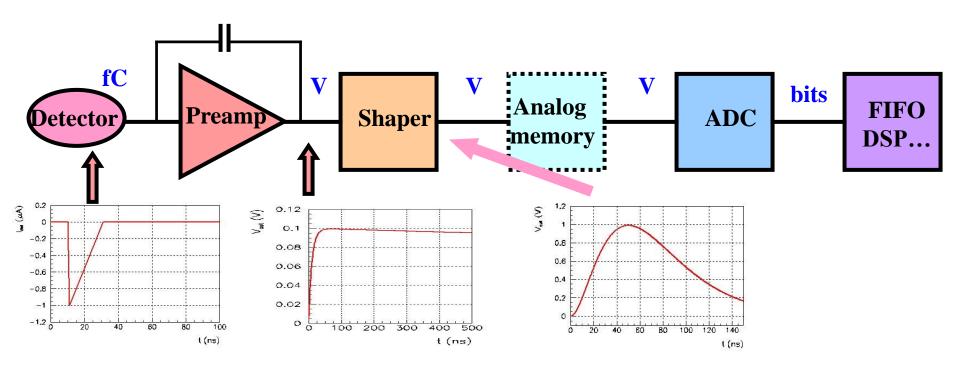
Most front-ends follow a similar architecture



- Very small signals (fC) -> need amplification
- Measurement of amplitude and/or time (ADCs, discris, TDCs)
- Several thousands to millions of channels
- Trends: high speed, low power

## Readout electronics : requirements



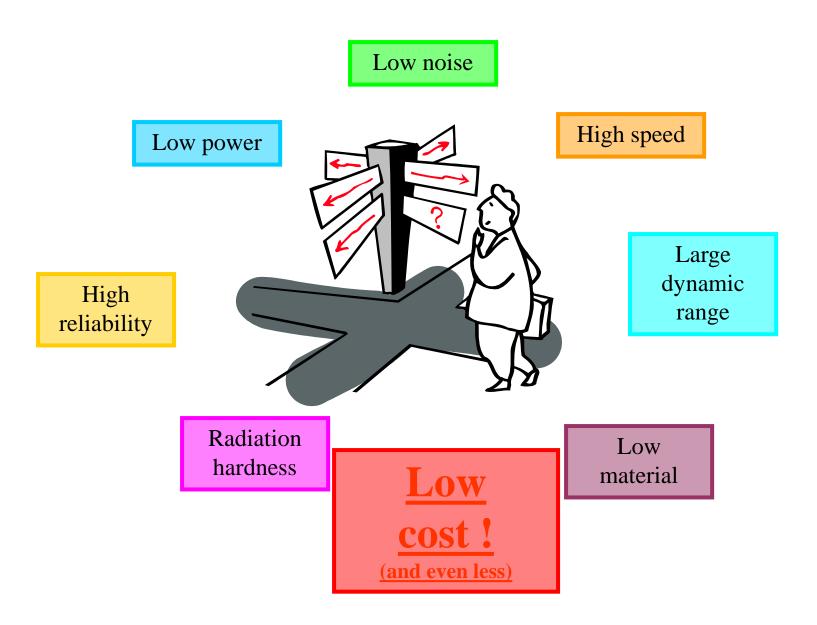

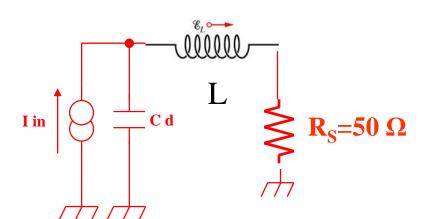
#### **Modelizing the sensor**

**O**mega


- Vacuum Photomultipliers
- $G = 10^5 10^7$
- Cd ~ 10 pF
- L ~ 10 nH








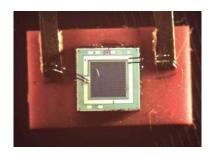- Silicon Photomultipliers
- $G = 10^5 10^7$
- C = 10 400 pF
- L = 1 10 nH



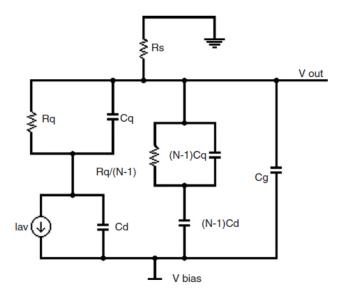


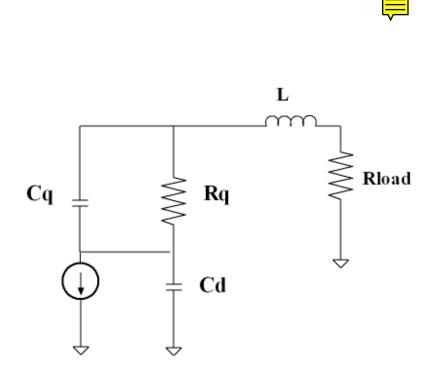
# **SiPM** impedance and model



 RLC too simple, inaccurate at high frequency

- C<sub>d</sub>R<sub>q</sub>C<sub>q</sub>LR OK
  - May better explain HF noise behaviour



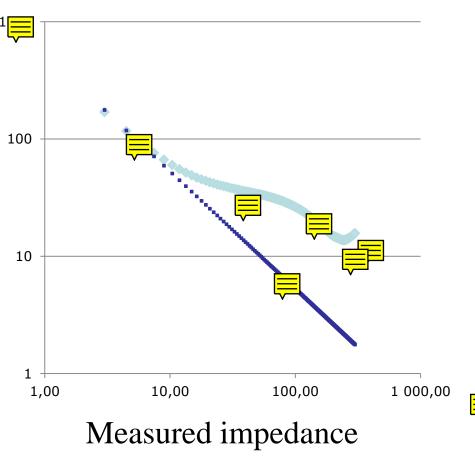

Measured impedance MPPC HPK 3x3 mm


Line : C = 320 pF


## Reading the signal


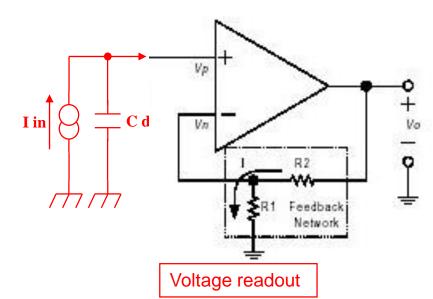
#### Signal

- Signal = current source
- Detector = capacitance C<sub>d</sub>
- Quantity to measure
- Charge => integrator needed
- Time => discriminator + TDC
- Integrating on Cd
  - Simple :  $V = Q/C_d \rightleftharpoons$
  - « Gain » :  $1/C_d$  : 1 pF -> 1 mV/fC
  - Need a follower to buffer the voltage...=> parasitic capacitance
  - Gain loss, possible non-linearities
  - crosstalk
  - Need to empty Cd…
- Exercise : calculate BW with opamp



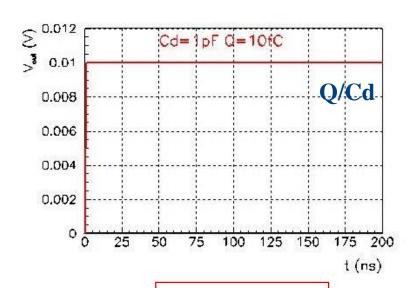

Impulse response

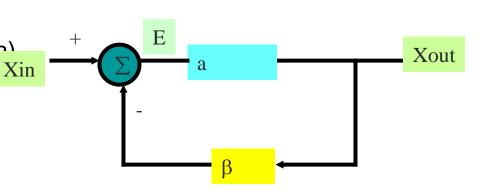
#### Feedback: an essential tool




- Improves gain performance
  - Less sensitivity to open loop gain (2)
  - Better linearity



- Potentially unstable
- Feedback constant : β = E/Xout
- Open loop gain : a = Xout/E
- Closed loop gain : Xout/Xin -> 1/β
- Loop gain :  $T = a\beta$



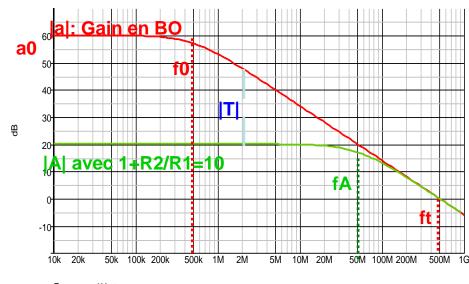
$$\frac{Xout}{Xin} = \frac{a}{1 + a\beta} = \frac{1/\beta}{1 + 1/a\beta}$$


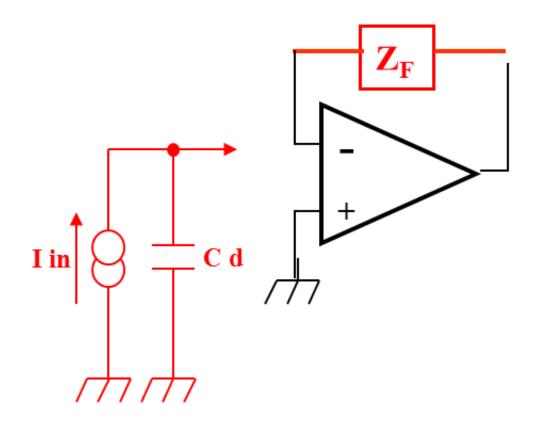
# **Transimpedance configuration**




- Calculate transimpedance
- Calculate β = Vin-/Vout and graphically BW



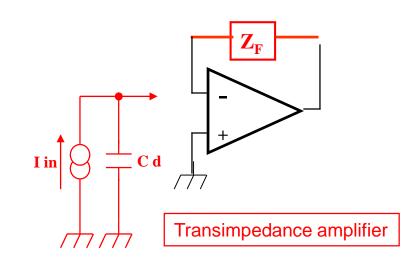
## **Transimpedance configuration**



- Transfer function
  - Using a VFOA with gain G
    - $V_{out} V_{in} = Z_f i_f$
    - $V_{in} = Z_d (i_{in} i_f) = V_{out}/G$
  - $V_{out}(\omega)/i_{in}(\omega) = -Z_f/(1 + Z_f/GZ_d)$
- $Zf = Rf / (1 + j\omega RfCf)$ 
  - At f << 1/2πRfCf :  $V_{out}(\omega)/i_{in}(\omega) = -R_f$ current preamp
  - At f << 1/2πRfCf :  $V_{out}(\omega)/i_{in}(\omega) = -1/j\omega C_f$  charge preamp
- Ballistic defict with charge preamp
  - Effect of finite gain : G<sub>0</sub>
  - Output voltage «only» Q C<sub>d</sub>/G<sub>0</sub>C<sub>f</sub>




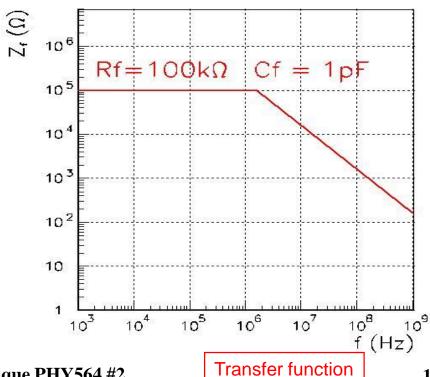
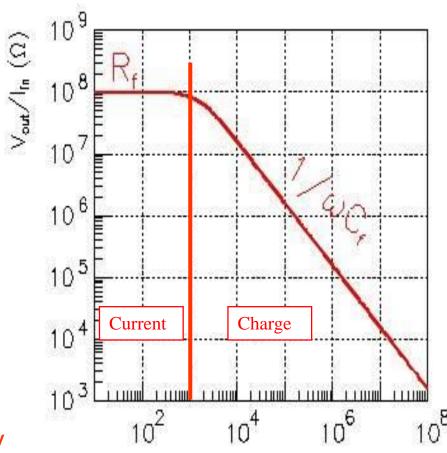
# **Charge vs Current preamps**



- Charge preamps
  - Best noise performance
  - Best with short signals
  - Best with small capacitance
- Current preamps
  - Best for long signals
  - Best for high counting rate
  - Significant parallel noise
- Charge preamps are <u>not slow</u>, they are <u>long</u>
- Current preamps are <u>not faster</u>, they are <u>shorter</u> (but easily unstable)



f(Hz)


# Input impedance




- Input impedance
  - Zin = Zf / G+1
  - Zin->0 virtual ground
  - Minimizes sensitivity to detector impedance
  - Minimizes crosstalk
- Equivalent model

$$- G(\omega) = G_0/(1 + j \omega/\omega_0)$$

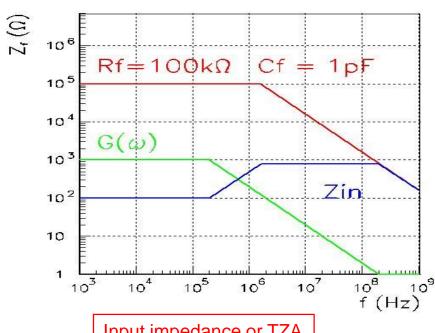- Terms due to Cf
  - $Zin = 1/j\omega G_0C_f + 1/G_0\omega_0 C_f$
  - Virtual resistance : Req =  $1/G_0\omega_0$  C<sub>f</sub>
- Terms due to Rf
  - $Zin = R_f/G_0 + j \omega R_f/G_0\omega_0$
  - Virtual inductance : Leq =  $R_f/G_0\omega_0$
- Possible oscillatory behaviour with capacitive source



Input impedance or TZA

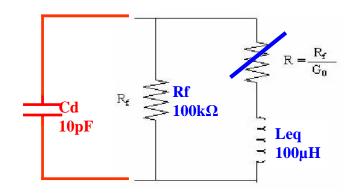


Equivalent circuit at the input
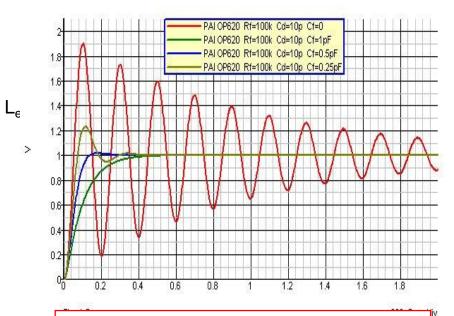
## **Current preamplifiers:**




- Easily oscillatory
  - Unstable with capacitive detector
  - Inductive input impedance : =  $R_f / \omega_C$
  - Resonance at :  $f_{res} = 1/2\pi \sqrt{L_{eq}C_d}$
  - Quality factor : Q = R /  $\sqrt{L_{eq}/C_d}$ 
    - Q > 1/2 -> ringing
  - Damping with capacitance C<sub>f</sub>
    - $C_f=2 \sqrt{(C_d/R_f G_0\omega_0)}$
    - Easier with fast amplifiers
- In frequency domain
  - $H(j\omega) = -Rf / (1 + j\omega RfC_d/G(\omega))$
  - $G(\omega) = G_0 / (1+j\omega/\omega_0)$

$$H = -Rf / (1 + j\omega R_f C_d / G_0 - \omega^2 R_f C_d / G_0 \omega_0)$$



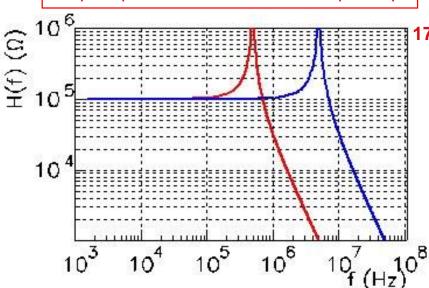
Step response of current sensitive preamp


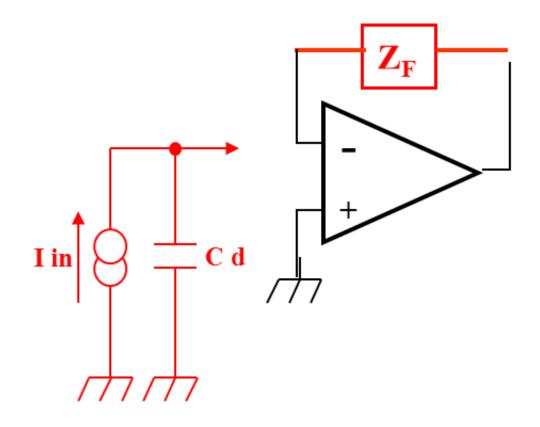
# **Signal integrity**




- Determine the current path...
- Effect of inductors in various parts



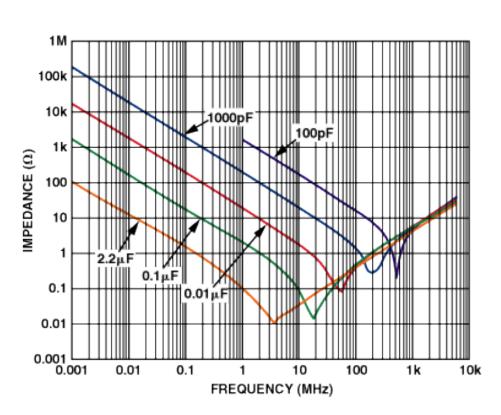
## **Decoupling capacitors**




- Exhibit parasitic resistance (ESR) and inductance
- Pay attention to components and PCB layout



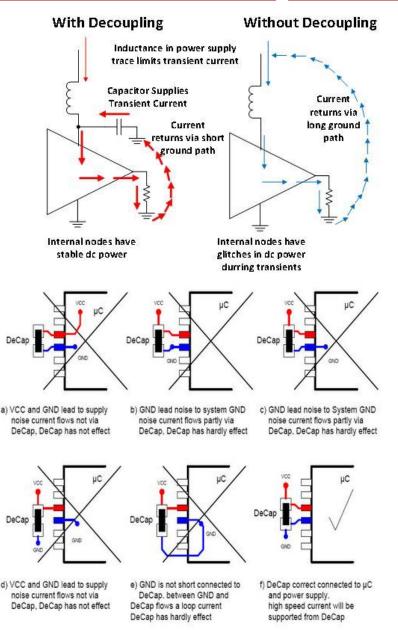




Radiated and conducted noise

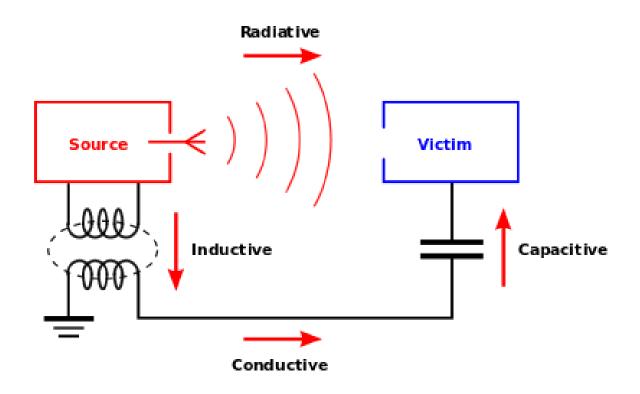


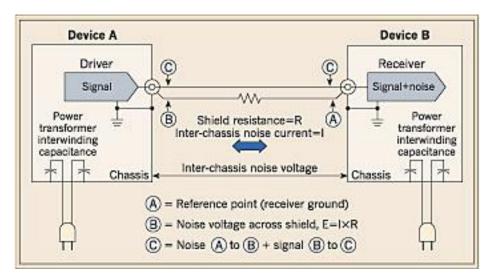
# Coupling by common impedance



- Parasitic signals from ground/substrate currents
- Star configuration (Single Ground Point) for DC or low frequency



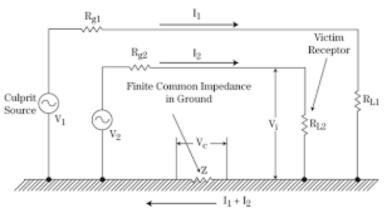


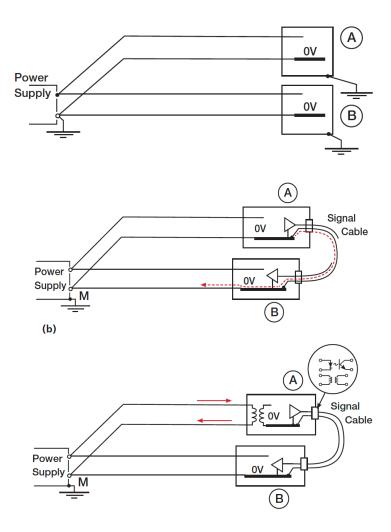
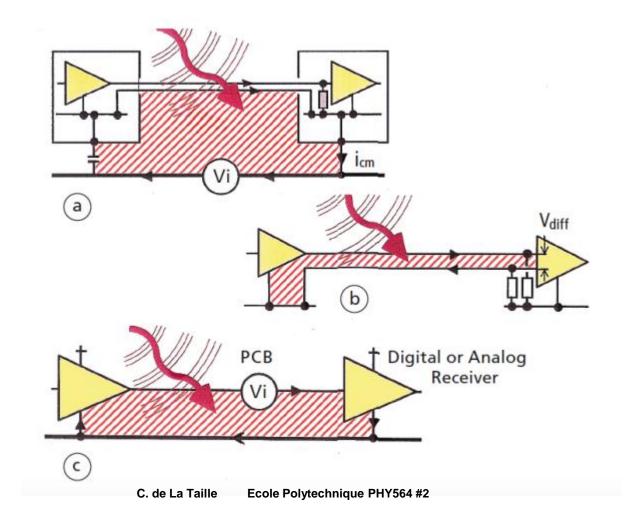
## Pick-up noise




- Noise coupling in loops
  - Reduce loop area, use coax or twisted pairs in long distances
  - Avoid floating the shield « breaking the ground loop » : works only at very low frequency


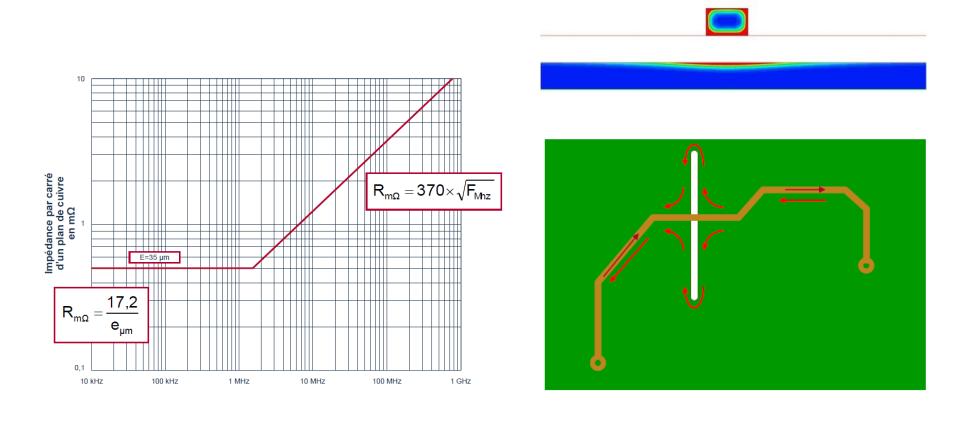
### **Ground impedance**




- Ground plane impedance, current return, ground slit = 1 nH/mm
- Line impedance :  $R = 0.5 \text{ L/W m}\Omega$  L = 1 nH/mm
- Skin depth :  $\delta \sim 2 / \sqrt{F(GHz)}$  (µm) (1 GHz = 2 µm)




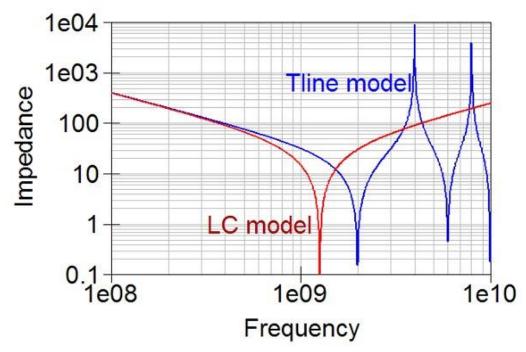
#### **Transmission lines**



- Ideal line: R = 0, G = 0
  - Characteristic impecance : Zc = sqrt(L/C)
  - Delay: td = sqrt(LC)
  - Speed depends only on dielectric  $v = c/\sqrt{\epsilon_r}$
  - delay td = L / v, typically 5 ns/m (FR4)
- Real line : R  $\neq$  0 and R( $\omega$ )



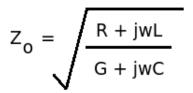

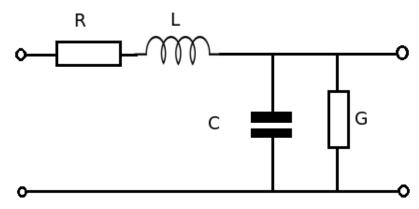

Equivalent circuit per unit length

R is resistance of wire/track

L is the inductance


C is the capacitance


G is the conductance of the dielectric


#### **Transmission lines**




#### Strip lines, microstrip

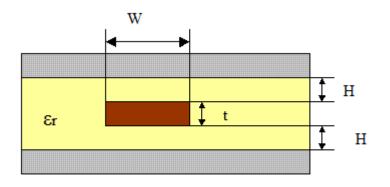

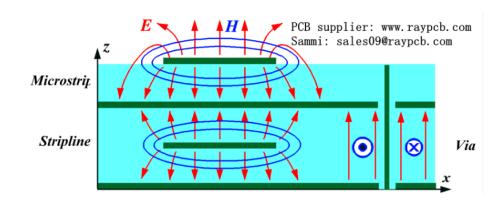


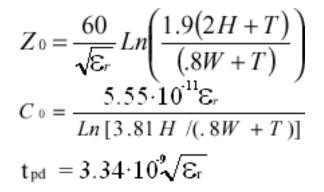

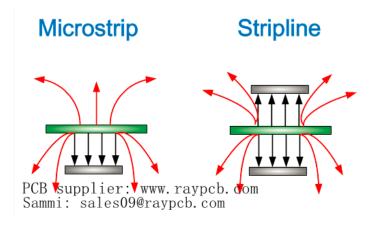


#### **Crosstalk between lines**




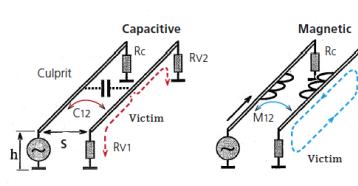

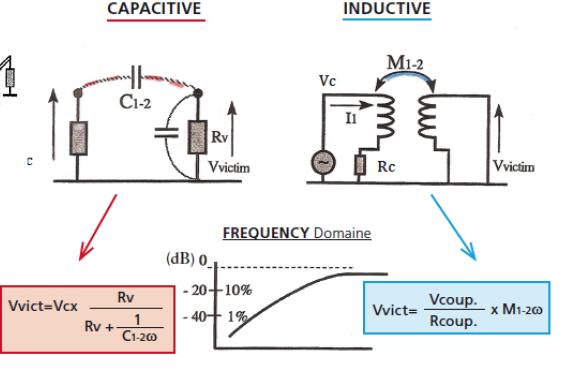- Capacitive/inductive coupling
  - Capacitive as dV/dt
  - Inductive as dl/dt
- Capacitive coupling easier to shield
- Prefer microstrip lines
- Rule of thumb :
  - Spacing = 5 \* distance to ground plane




Vvict= Rv C1-2 ΔV/Δt

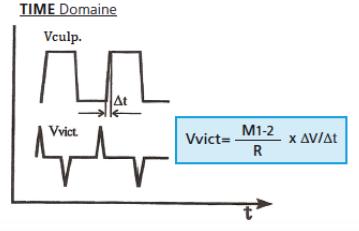
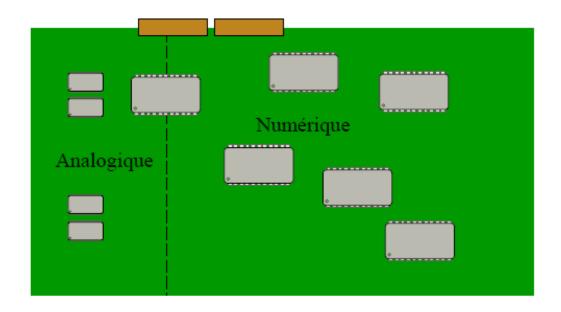
# Mixed signal boards



- Component placement
  - Separate analog and digital parts
  - Place analog on one side
  - Bring power supplies from the digital side
- Ground management
  - Use a common ground plane analog/digital
  - Avoid ground splits



## Field bus




- GPIB
- |2C
- CAN
- JTAG
- USB
- Ethernet
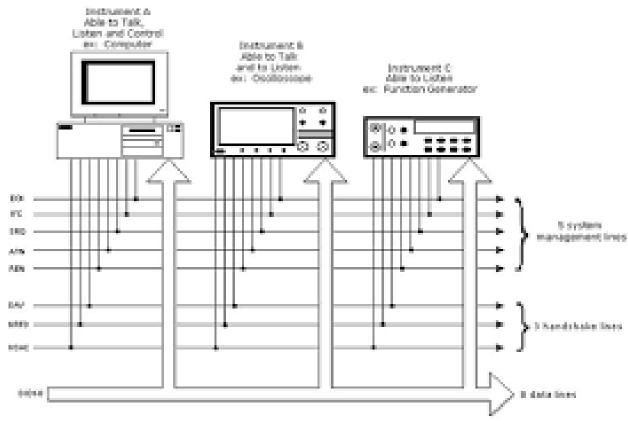
#### **GPIB** bus



- General Purpose Interface Bus IEEE488 1975
  - Connection between computer and measurement apparatus
  - Bi-directional, asynchronous, 8bits parallel,
  - 1 Mbyte/s, 24 instruments, 20 m open collector 5 V
  - Instruments (slaves) are controlled by the computer (master)






# **GPIB** bus description

**O**mega


- 8 data lines (OC)
- 3 control lines (OC): DAV (data valid), NRFD (not ready for data), NDAC (no data accepted)
- 5 management lines: ATN, IFC, REN, SRQ, EOI

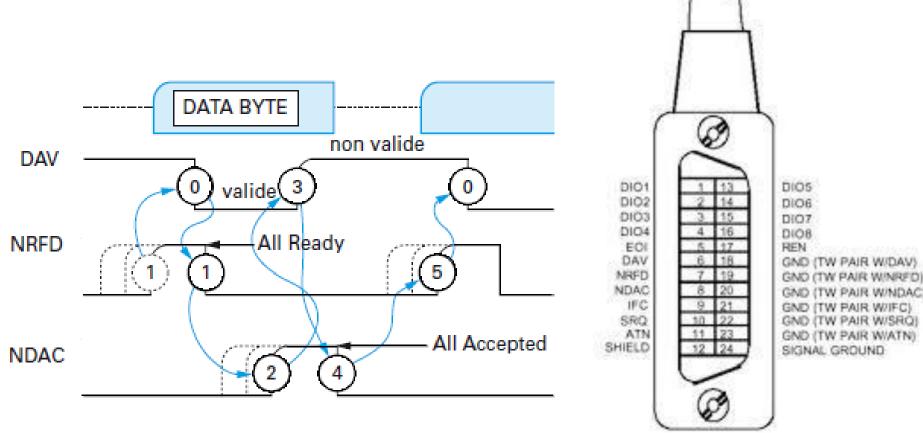• No conflicts possible: instruments talk only when requested to do so






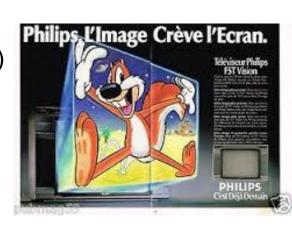- Inter Integrated Circuits
  - Connection between chips in televisions (Philips 1982)
  - Bidirectionnal, synchronous, 8 bits serial
  - 2 lines : SDA (serial data) and SCL (serial clock)
  - 400 kb/s, 1024 instruments



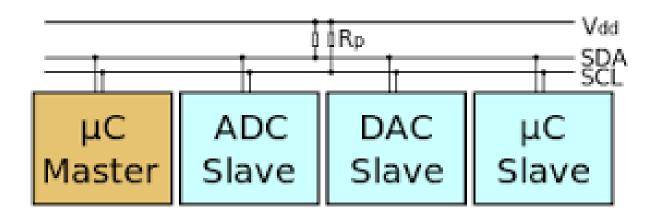- Conflit management
  - Any circuit can broadcast when the line is free
  - In case of collisions, the most important recipient (lowest address) is prioritary





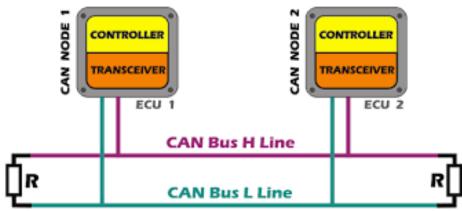
#### **CAN** bus



- Controller Area Network (Bosch Gmbh 1983)
  - Serial bus to reduce amount of cables in cars
  - Bi-directionnal, synchronous, serial 100 bits
  - 2 wires 100  $\Omega$  line, 1 Mbits/s, 64 circuits, 2048 messages, 1 km
- Conflit management
  - Any circuit can broadcast when the line is free
  - In case of collisions, the most important message is prioritary





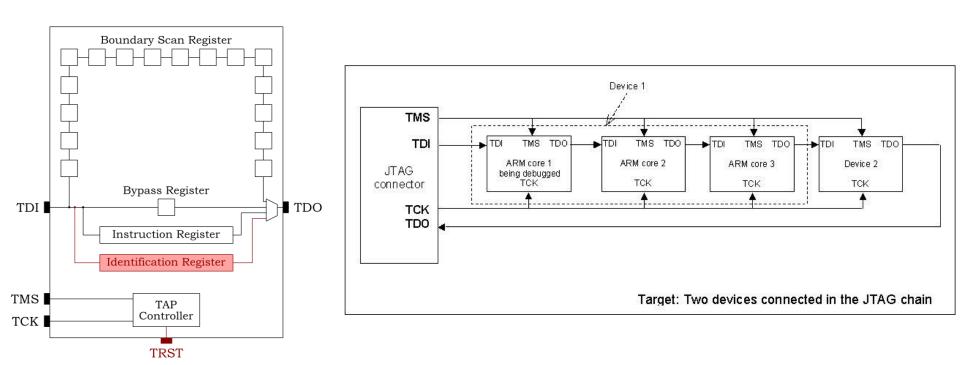
#### **JTAG**




- Join Test Action Group (1990) IEEE 1149.1
  - Goal : probeless test of digital Ics on a PCB (boundary scan)
  - Unidirectional, synchronous, serial, 5 lines, 50 Mbit/s
  - 5 lines : TDI (test data in) TDO (test data out) TMS (test mode select)
    TCK (clock) TRST\* (resetb)


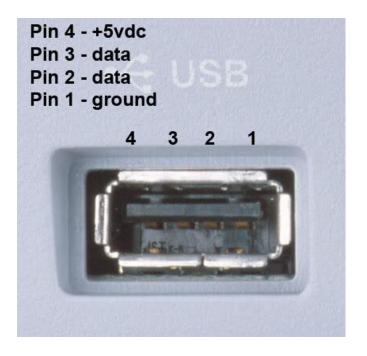
#### **USB**




- Universal Serial Bus (1996)
  - goal : replace various incompatible I/O ports on computers
  - USB1 (96): 12 Mb/s, USB2 (01): 480 Mb/s, USB3 (08) 4.8 Gb/s
  - Low cost, wide use, power service 5 V 500 mA
  - High rate, autodetection of devices, hot plug&play
  - Up to 127 devices per computer, but limited to 5 m
- Architecture : master/slave
  - tree-based (host), point to point connection
  - 3 transfer types : isochronous, interrupt, bulk


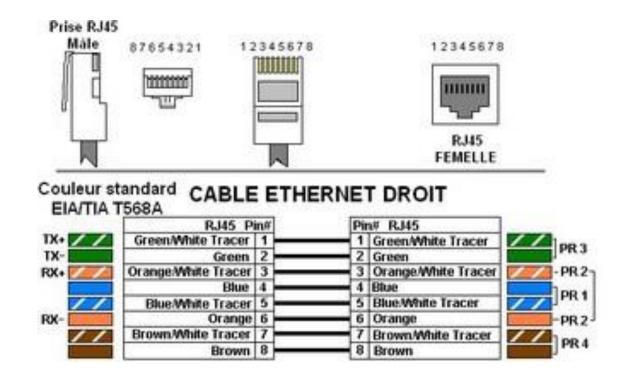
#### **Ethernet**



- Network connection for computers (1985) IEEE 802.3
  - Created in 1970, normalized in 1985
  - Unique MAC address, serial transmission (frames)
  - Coaxial cable or twisted pairs, optical fiber or wireless
  - CSMA-CD : Carrier Sense (listen before talking) Multiple Access (anyone can talk) Collision Detection (detect multiple talkers)






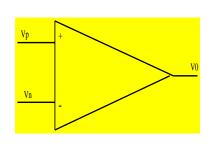
## **Amplifiers : a large zoo**

**O**mega

- Voltage feedback operationnal amplifier (VFOA)
- Voltage amplifiers, RF amplifiers (VA,LNA)
- Current feedback operationnal amplifiers (CFOA)
- Current conveyors (CCI, CCII +/-)
- Current (pre)amplifiers (ISA,PAI)
- Charge (pre)amplifiers (CPA,CSA,PAC)
- Transconductance amplifiers (OTA)
- Transimpedance amplifiers (TZA,TIA, OTZ)
- Mixing up open loop (OL) and closed loop (CL) configurations!




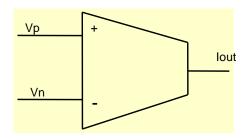
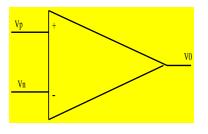
# Only 4 open-loop configurations




- Voltage operationnal amplifiers (OA, VFOA)
  - Vout =  $G(\omega)$  Vin diff
  - Zin+ = Zin- = ∞ Zout = 0




- Transimpedance operationnal amplifier (CFOA!)
  - Vout =  $Z(\omega)$  iin
  - Zin- = 0

Zout = 0

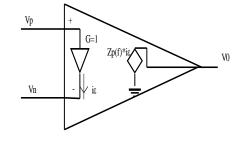

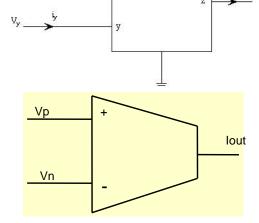
- Current conveyor (CCI,CCII)
  - lout =  $G(\omega)$  lin
  - Zin = 0
- Zout = ∞
- Transconductance amplifier (OTA)
  - Iout =  $Gm(\omega)$  Vin diff
  - Zin+ = Zin- = ∞ Zout = ∞


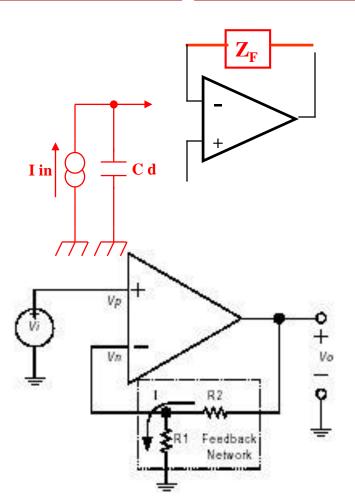
# Only 4 feedback configurations




- Shunt-shunt = transimpedance
  - Small Zin (= Zin(OL)/T) -> current input
  - small Zout (= Zout(OL)/T) -> voltage output
  - De-sensitizes transimpedance =  $1/\beta = Zf$
- Series-shunt
  - Large Zin (= Zin(OL)\*T) -> voltage input
  - Small Zout (= Zout(OL)/T) -> voltage output
  - Optimizes voltage gain (=  $1/\beta$ )
- Shunt series
  - Small Zin (= Zin(OL)/T) -> current input
  - Large Zout (= Zout(OL)\*T) -> current output
  - Current conveyor
- Series-series
  - Large Zin (= Zin(OL)\*T) -> voltage input
  - Large Zout (= Zout(OL)\*T) -> current output
  - Transconductance
  - Ex : common emitter with emitter degenration


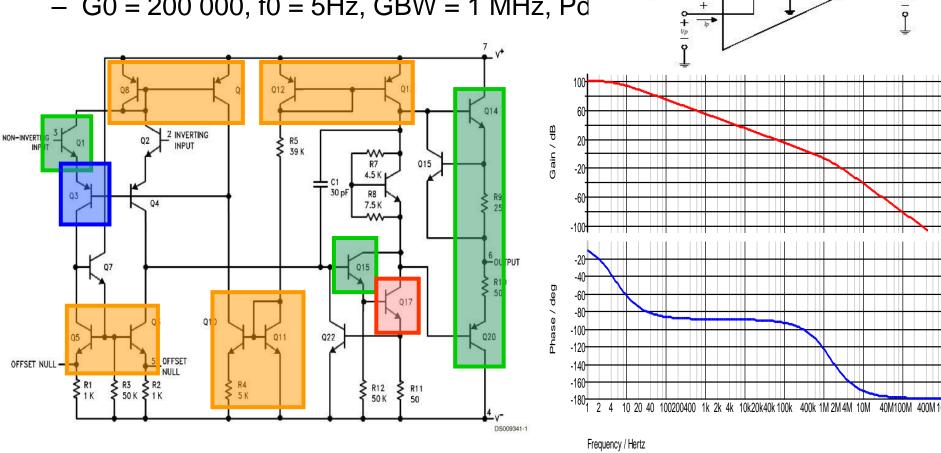
# **Voltage Feedback Operationnal Amplifiers (1)**



- Back to the 70's: LM741
  - 3 stages : Paraphase=CE, Darlington=CE,
  - $G0 = 200\ 000, f0 = 5Hz, GBW = 1 MHz, Pd$



Schematic diagramm of a LM741 (1970) **©National Semiconductors** 


# **Voltage Feedback Operationnal Amplifiers (2)**





- Breakthrough in the 90's: OP620-621
  - 2 stages :Cascode=CE, Push-pull= CC
  - Pd = 250 mW
  - G0 = 1000

Frequency / Hertz

- f0 = 500kHz

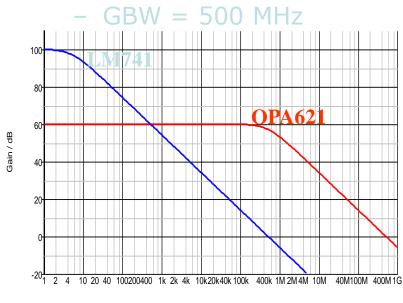

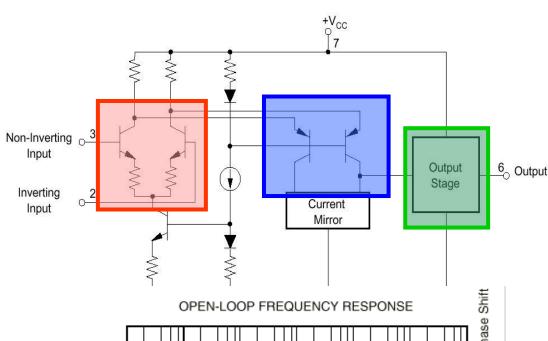

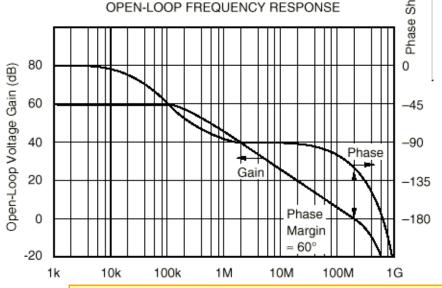


Open loop frequency response of OP620
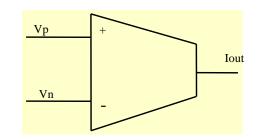
# **Transconductance amplifier (OTA)**

**O**mega

- Voltage input : large Zin
- Current output : large Zout
- V2I conversion : Iout= Gm(ω) Vin diff



- Differential pair for voltage to current conversion
- Active load for differential to unipolar
- Current mirrors for symmetrical output

